

# Carry Look Ahead Adder Subtractor

## Half Adder – Design Source File

---

```
-- Group 17
-- Senevirathne S.M.P.U.
--
-- Create Date: 04/16/2024 12:02:05 PM
-- Design Name: Carry_Look_Ahead_Adder_Subtractor
-- Module Name: Half_Adder - Behavioral
-- Project Name: Nanoprocessor
-- Target Devices: Basys3 Board
```

---

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Half_Adder is
    Port ( A : in STD_LOGIC; --First input bit
          B : in STD_LOGIC; --Second input bit
          Sum : out STD_LOGIC; --Sum output bit
```

```

        Carry : out STD_LOGIC); --Carry output bit
end Half_Adder;

```

architecture Behavioral of Half\_Adder is

```
begin
```


```
    --Defining sum and carry of the half adder
```

```
    Sum <= A XOR B;
```

```
    Carry <= A AND B;
```

```
end Behavioral;
```

## Half Adder – Design Schematic

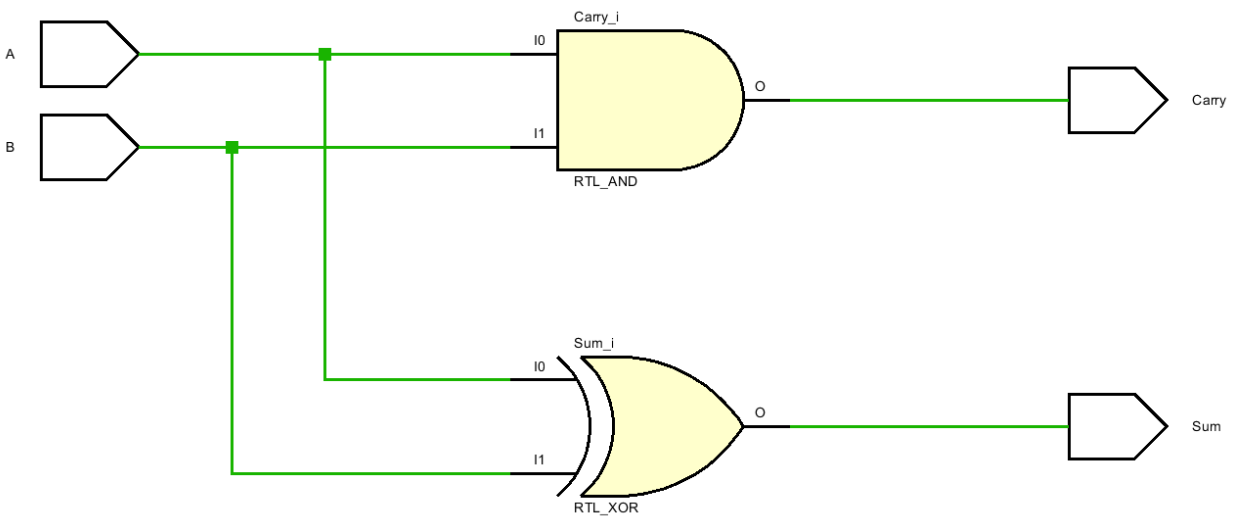

## Full Adder – Design Source File

-----

-- Group 17  
-- Senevirathne S.M.P.U.  
--  
-- Create Date: 04/16/2024 12:27:08 PM  
-- Design Name: Carry\_Look\_Ahead\_Adder\_Subtractor  
-- Module Name: Full\_Adder - Behavioral  
-- Project Name: Nanoprocessor  
-- Target Devices: Basys3 Board

-----  
  
library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity Full\_Adder is

Port ( A : in STD\_LOGIC; --First input bit

B : in STD\_LOGIC; --Second input bit

Carry\_in : in STD\_LOGIC; --Carry input bit

Sum : out STD\_LOGIC; --Sum output bit

Carry\_out : out STD\_LOGIC; --Carry output bit

P : out STD\_LOGIC; --Propergate output bit

G : out STD\_LOGIC); --Generate output bit

end Full\_Adder;

architecture Behavioral of Full\_Adder is

component Half\_Adder

Port ( A : in STD\_LOGIC; --First input bit

B : in STD\_LOGIC; --Second input bit

Sum : out STD\_LOGIC; --Sum output bit

```

    Carry : out STD_LOGIC); --Carry output bit
end component;

SIGNAL A1, A2, B1, B2: std_logic; --signal inputs of the two half adders
SIGNAL Sum1, Sum2, Carry1, Carry2: std_logic; --signal outputs of the two half adders
begin
    Half_Adder_2 : Half_Adder --mapping the bottom half adder
    port map(
        A => A2,
        B => B2,
        Sum => Sum2,
        Carry => Carry2
    );
    Half_Adder_1 : Half_Adder --mapping the top half adder
    port map(
        A => A1,
        B => B1,
        Sum => Sum1,
        Carry => Carry1
    );
    --Assigning the inputs to the bottom half adder
    A2 <= A;
    B2 <= B;

    --Defining generation and propagation bits
    P <= Sum2;
    G <= Carry2;

    --Assigning the inputs to the top half adder

```

```
B1 <= Carry_in;
```

```
A1 <= Sum2;
```


```
--Defining Carry_out and sum
```

```
Carry_out <= Carry2 OR Carry1;
```

```
Sum <= Sum1;
```

```
end Behavioral;
```

## Full Adder – Design Schematic

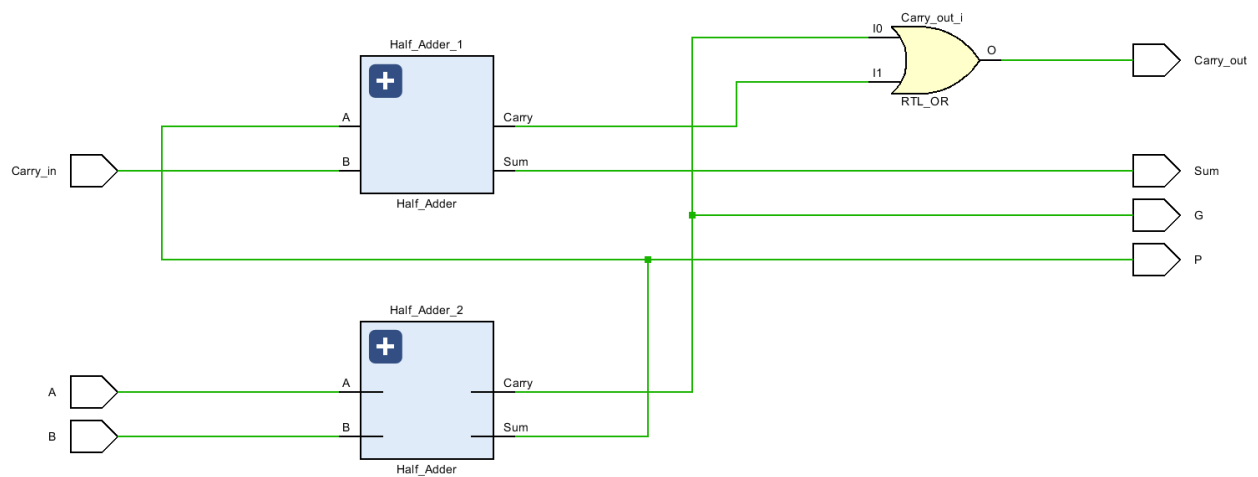

## Carry Look Ahead Logic – Design Source File

```
-- Group 17
```

```
-- Senevirathne S.M.P.U.
```

```
--
```

```
-- Create Date: 04/16/2024 01:35:19 PM
```

```
-- Design Name: Carry_Look_Ahead_Adder_Subtractor
-- Module Name: Carry_Look_Ahead - Behavioral
-- Project Name: Nanoprocessor
-- Target Devices: Basys3 Board
```

-----

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Carry_Look_Ahead is
```

```
    Port ( P : in STD_LOGIC_VECTOR (2 downto 0); --Propergate input bus
```

```
          G : in STD_LOGIC_VECTOR (2 downto 0); --Propergate output bus
```

```
          Carry_in : in STD_LOGIC; --Carry input bit
```

```
          Carry_out : out STD_LOGIC_VECTOR (3 downto 2)); --Carry output bus
```

```
end Carry_Look_Ahead;
```

```
architecture Behavioral of Carry_Look_Ahead is
```

```
begin
```

```
--Defining Carry_out(2)
```


```
Carry_out(2) <= (Carry_in AND P(0) AND P(1)) OR (G(0) AND P(1)) OR G(1);
```

```
--Defining Carry_out(1)
```

```
Carry_out(3) <= (Carry_in AND P(0) AND P(1) AND P(2)) OR (G(0) AND P(1) AND P(2)) OR (G(1) AND P(2)) OR G(2);
```

```
end Behavioral;
```
 
## Carry Look Ahead Logic – Design Schematic



## Carry Look Ahead Adder Subtractor – Design Source File

```
-----  
  
-- Group 17  
-- Senevirathne S.M.P.U.  
--  
-- Create Date: 04/16/2024 02:13:42 PM  
-- Design Name: Carry_Look_Ahead_Adder_Subtractor  
-- Module Name: Carry_Look_Ahead_Adder_Subtractor - Behavioral  
-- Project Name: Nanoprocessor  
-- Target Devices: Basys3 Board  
  
-----
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Carry_Look_Ahead_Adder_Subtractor is
```

```
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0); --Bus for the first binary number
```

```

    B : in STD_LOGIC_VECTOR (3 downto 0); --Bus for the second binary number

    Add_Sub : in STD_LOGIC; --Should we add B to A or should we subtract B from A? (1 for
subtraction, 0 for addition)

    EN : in STD_LOGIC; --Enable input

    S : inout STD_LOGIC_VECTOR (3 downto 0); --Bus for the binary sum output

    Sign : inout STD_LOGIC; --Sign Bit: 1 for negative, 0 for positive

    Overflow : inout STD_LOGIC; --Overflow bit: Is there an overflow?

    --When the number is negative, is the number in range [-0,-8]: if yes, there is no overflow =>
Overflow =0; if no, there is an overflow => Overflow = 1

    --When the number is positive, is the number in range [+0, 7]: if yes, there is no overflow =>
Overflow =0; if no, there is an overflow => Overflow = 1

    Zero : out STD_LOGIC; --Is the output zero(0000)?
end Carry_Look_Ahead_Adder_Subtractor;

```

architecture Behavioral of Carry\_Look\_Ahead\_Adder\_Subtractor is  
component Full\_Adder is

```

Port ( A : in STD_LOGIC; --First input bit

    B : in STD_LOGIC; --Second input bit

    Carry_in : in STD_LOGIC; --Carry input bit

    Sum : out STD_LOGIC; --Sum output bit

    Carry_out : out STD_LOGIC; --Carry output bit

    P : out STD_LOGIC; --Propergate output bit

    G : out STD_LOGIC; --Generate output bit

end component;

```

component Carry\_Look\_Ahead is

```

Port ( P : in STD_LOGIC_VECTOR (2 downto 0); --Propergate input bus

    G : in STD_LOGIC_VECTOR (2 downto 0); --Propergate output bus

    Carry_in : in STD_LOGIC; --Carry input bit

    Carry_out : out STD_LOGIC_VECTOR (3 downto 2)); --Carry output bus

```



```
end component;
```

```
--Signal the inputs and outputs of internal components
```

```
SIGNAL A0, B0, C1, P0, G0: std_logic; --FA0
```

```
SIGNAL A1, B1, P1, G1: std_logic; --FA1
```

```
SIGNAL A2, B2, C2, P2, G2: std_logic; --FA2
```

```
SIGNAL A3, B3, C3: std_logic; --FA3
```

```
--An and Bn are n th bits of the binary numbers A and B inserted to the relevant(n th) Full Adder
```

```
--Cn is the carry bit generated by adding the n th bits of A and B
```

```
--Pn and Gn are propagation and generation bits of the relevant(n th) Full Adder
```

```
begin
```

```
Full_Adder_0 : Full_Adder --mapping first full adder
```

```
    port map(A => A0,
```

```
            B => B0,
```

```
            Carry_in => Add_Sub, --C0
```

```
            Sum => S(0),
```

```
            Carry_out => C1,
```

```
            P => P0,
```

```
            G => G0
```

```
);
```

```
Full_Adder_1 : Full_Adder --mapping second full adder
```

```
    port map(A => A1,
```

```
            B => B1,
```

```
            Carry_in => C1,
```

```
            Sum => S(1),
```

```
            P => P1,
```

```
            G => G1
```

```
);
```

Full\_Adder\_2 :Full\_Adder --mapping third full adder

port map(A => A2,

B => B2,

Carry\_in => C2,

Sum => S(2),

P => P2,

G => G2

);

Full\_Adder\_3 :Full\_Adder --mapping last full adder

port map(A => A3,

B => B3,

Carry\_in => C3,

Sum => S(3),

Carry\_out => Sign --carry output of the Carry Look Ahead Adder Subtractor

);

Carry\_Look\_Ahead\_0 : Carry\_Look\_Ahead --mapping carry look ahead logic unit

port map(P(0) => P0, P(1) => P1, P(2) => P2,

G(0) => G0, G(1) => G1, G(2) => G2,

Carry\_in => Add\_Sub, --C0

Carry\_out(2) => C2, Carry\_out(3) => C3

);

--Defining inputs of FA0 (A0, B0)

A0 <= A(0) AND EN;

B0 <= (EN AND B(0)) XOR Add\_Sub;

--Defining inputs of FA1 (A1, B1)

A1 <= A(1) AND EN;

B1 <= (EN AND B(1)) XOR Add\_Sub;

--Defining inputs of FA2 (A2, B2)

$A2 \leq A(2) \text{ AND } EN;$

$B2 \leq (EN \text{ AND } B(2)) \text{ XOR Add\_Sub};$

--Defining inputs of FA3 (A3, B3)

$A3 \leq A(3) \text{ AND } EN;$

$B3 \leq (EN \text{ AND } B(3)) \text{ XOR Add\_Sub};$

--Defining the overflow bit


$\text{Overflow} \leq C3 \text{ XOR Sign};$

--Defining the zero flag


$\text{Zero} \leq EN \text{ AND NOT}(S(0) \text{ OR } S(1) \text{ OR } S(2) \text{ OR } S(3));$

end Behavioral;
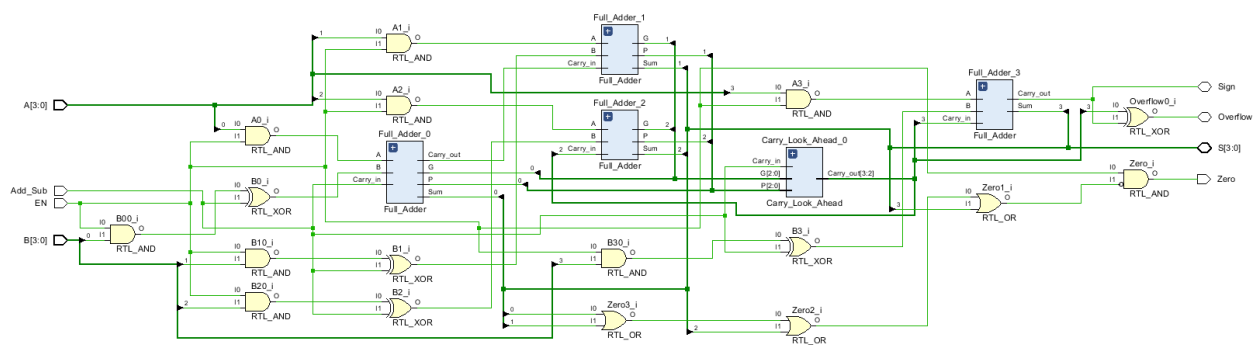
## Carry Look Ahead Adder Subtractor – Design Schematic


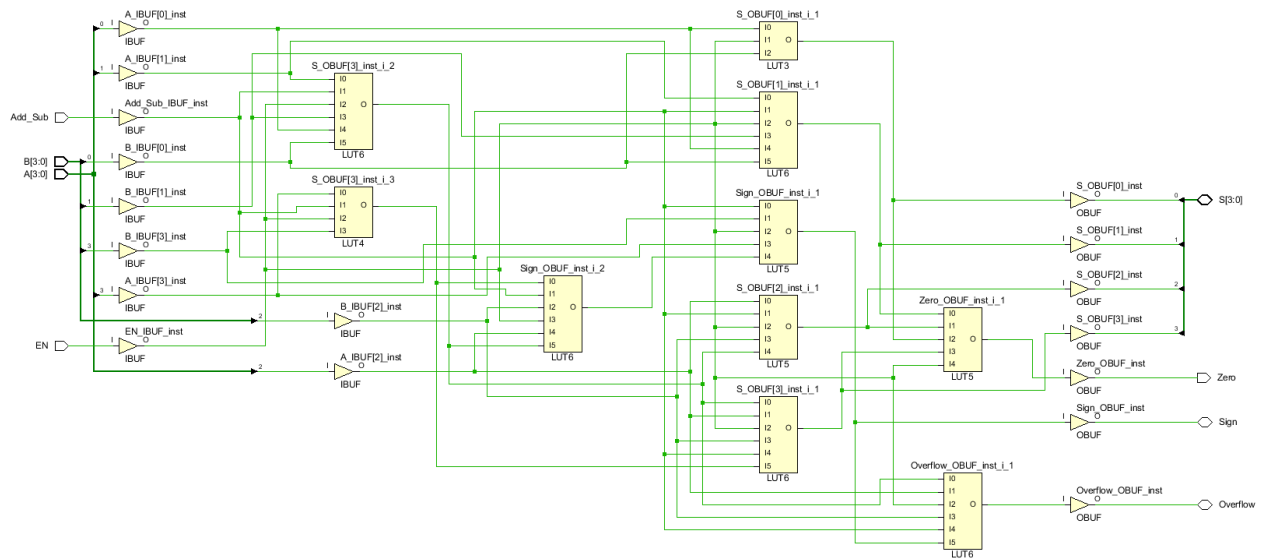
# Carry Look Ahead Adder Subtractor – Implemented Design Schematic



## Carry Look Ahead Adder Subtractor – Simulation File

-----

-- Group 17

-- Senevirathne S.M.P.U.

--

-- Create Date: 04/16/2024 04:38:31 PM

-- Design Name: Carry\_Look\_Ahead\_Adder\_Subtractor

-- Module Name: Carry\_Look\_Ahead\_Adder\_Subtractor\_TB - Behavioral

-- Project Name: Nanoprocessor

-- Target Devices: Basys3 Board

-----

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Carry_Look_Ahead_Adder_Subtractor_TB is
```

```
end Carry_Look_Ahead_Adder_Subtractor_TB;
```

```
architecture Behavioral of Carry_Look_Ahead_Adder_Subtractor_TB is
```

```
    component Carry_Look_Ahead_Adder_Subtractor is
```

```
        Port ( A : in STD_LOGIC_VECTOR (3 downto 0); --Bus for the first binary number
```

```
              B : in STD_LOGIC_VECTOR (3 downto 0); --Bus for the second binary number
```

```
              Add_Sub : in STD_LOGIC; --Should we add B to A or should we subtract B from A? (1 for subtraction, 0 for addition)
```

```
              EN : in STD_LOGIC; --Enable input
```

```
              S : inout STD_LOGIC_VECTOR (3 downto 0); --Bus for the binary sum output
```

```
              Sign : inout STD_LOGIC; --Sign Bit: 1 for negative, 0 for positive
```

```
              Overflow : inout STD_LOGIC; --Overflow bit: Is there an overflow?
```

```
              --When the number is negative, is the number in range [-0,-8]: if yes, there is no overflow => Overflow =0; if no, there is an overflow => Overflow = 1
```

```
              --When the number is positive, is the number in range [+0, 7]: if yes, there is no overflow => Overflow =0; if no, there is an overflow => Overflow = 1
```

```
              Zero : out STD_LOGIC; --Is the output zero(0000)?
```

```
    end component;
```

```
    --Signal the inputs and outputs of Carry Look Ahead Adder Subtractor
```

```
    SIGNAL A, B, S : std_logic_vector(3 downto 0);
```

```
    SIGNAL Add_Sub, EN, Sign, Overflow, Zero: std_logic;
```

```
begin
```

```
    Carry_Look_Ahead_Adder_Subtractor_Sim : Carry_Look_Ahead_Adder_Subtractor --mapping Carry Look Ahead Adder Subtractor for simulation
```

```

port map(
    A => A,
    B => B,
    Add_Sub => Add_Sub,
    EN => EN,
    S => S,
    Sign => Sign,
    Overflow => Overflow,
    Zero => Zero
);

```

```

process begin
    wait for 100ns;

    EN <= '1';
    Add_Sub <= '0';
    A <= "0000";

    B <= "0000"; -- 0+0 = 0000(0), Carry = 0 (+0), Overflow = 0(C=0, positive; O=0, No overflow => in
range [+0,7] )

```

```

    wait for 100ns;

    A <= "1001";

    B <= "0010"; -- -7+(2) = -5 = 1011(d), Carry =1, Overflow =0 (C=1, negative; O= 1, No overflow =>
in range [-0,-8] )

```

```

    wait for 100ns;

    A <= "0110";

    B <= "0110"; -- 6+(6) = 12 = 1100(c), Carry =0, Overflow =1 (C=0, positive; O= 0, overflowed
positively => Above 7 )

```

```

    wait for 100ns;

```

A <= "0001";

B <= "0010"; --  $1+2 = 3 = 0011(3)$ , Carry = 0, Overflow = 0 (C=0, positive; O=0, No overflow => in range [+0,7] )

wait for 100ns;

A <= "1000";

B <= "0111"; --  $-8+7 = -1 = 1111(f)$ , Carry = 1, Overflow = 0 (C=1, negative; O=1, No overflow => in range [-0,-8] )

wait for 100ns;

A <= "0111";

B <= "1000"; --  $7+(-8) = -1 = 1111(f)$ , Carry = 1, Overflow = 0 (C=1, negative; O=1, No overflow => in range [-0,-8] )

wait for 100ns;

A <= "0111";

B <= "1001"; --  $7+(-7) = 0 = 0000(0)$ , Carry = 0 (+0), Overflow = 0 (C=0, positive; O=0, No overflow => in range [+0,7] )

wait for 100ns;

A <= "0100";

B <= "1101"; --  $4+(-3) = 1 = 0001(1)$ , Carry = 0, Overflow = 0 (C=0, positive; O=0, No overflow => in range [+0,7] )

wait for 100ns;

A <= "0100";

B <= "1100"; --  $4+(-4) = 0 = 0000(0)$ , Carry = 0 (+0), Overflow = 0 (C=0, positive; O=0, No overflow => in range [+0,7] )

wait for 100ns;

A <= "1001";

B <= "0001"; --  $-7+(1) = -6 = 1010(a)$ , Carry =1, Overflow =0 (C=1, negative; O= 0, No overflow => in range [-0,-8] )

wait for 100ns;

A <= "1001";

B <= "0010"; --  $-7+(2) = -5 = 1011(b)$ , Carry =1, Overflow =0 (C=1, negative; O= 0, No overflow => in range [-0,-8] )

wait for 100ns;

Add\_Sub <= '1';

A <= "0000";

B <= "0000"; --  $0-0 = 0000(0)$ , Carry = 1 (-0), Overflow = 0(C=1, negative; O=0, No overflow => in range [-0,-8])

wait for 100ns;

A <= "1001";

B <= "0010"; --  $-7-(2) = -9 = 0111(7)$ , Carry =1, Overflow =1 (C=1, negative; O= 1, overflowed negatively => Below -8 )

wait for 100ns;

A <= "0110";

B <= "0110"; --  $6-(6) = 0 = 0000(0)$ , Carry =1 (-0), Overflow =0 (C=1, negative; O= 0, No overflow => in range[-0-8] )

wait for 100ns;

A <= "0001";

B <= "0010"; --  $1-2 = -1 = 1111(f)$ , Carry = 1, Overflow = 0(C=1, negative; O=0, No overflow => in range [-0,-8])

wait for 100ns;

A <= "1000";



B <= "0111"; -- -8-7 = -15 = 0001(1), Carry = 1, Overflow = 1 (C=1, negative; O=1, overflowed negatively => Below -8)

wait for 100ns;

A <= "0111";

B <= "1000"; -- 7-(-8) = 15 = 1111(f), Carry = 0, Overflow = 1 (C=0, positive; O=1, overflowed positively => Above 7)

wait for 100ns;

A <= "0111";

B <= "1001"; -- 7-(-7) = 14 = 1110(e), Carry = 0, Overflow = 1 (C=0, positive; O= 1, overflowed positively => Above 7)

wait for 100ns;

A <= "0100";

B <= "1101"; -- 4-(-3) = 7 = 0111(7), Carry = 0, Overflow = 0 (C=0, positive; O= 0, No overflow => in range [+0,7] )

wait for 100ns;

A <= "0100";

B <= "1100"; -- 4-(-4) = 8 = 1000(8), Carry = 0, Overflow = 1 (C=0, positive; O= 0, overflowed positively => Above 7 )

wait for 100ns;

A <= "1001";

B <= "0001"; -- -7-(1) = -8 = 1000(8), Carry = 1, Overflow = 0 (C=1, negative; O= 0, No overflow => in range [-0,-8] )

wait for 100ns;

A <= "1001";

B <= "0010"; -- -7-(2) = -9 = 0111(7), Carry =1, Overflow =1 (C=1, negative; O= 1, overflowed negatively => Below -8 )

wait;

end process;

end Behavioral;

## Carry Look Ahead Adder Subtractor – Timing Diagram

